

EML Tut-6

$$K\phi = 1.44 \text{ V/rad/s}$$

$$R_a = 0.86 \Omega$$

$$I_a = 40 \text{ A}$$

Sol:

$$V_t = E_b + I_a R_a$$

$$E_b = K\phi \omega = 1.44 \times 150 = 216 \text{ V}$$


$$= 216 + 40 \times 0.86 = 250.4 \text{ V}$$

b) The no load speed

$$\omega_{\text{no-load}} = \frac{250.4}{1.44} = 173.88$$

2, $R_a = 0.4 \Omega$ $V = 200 \text{ V}$ $\omega = 500 \text{ rpm} = 52.35 \text{ rad/s}$

$$I_a = 25 \text{ A}$$

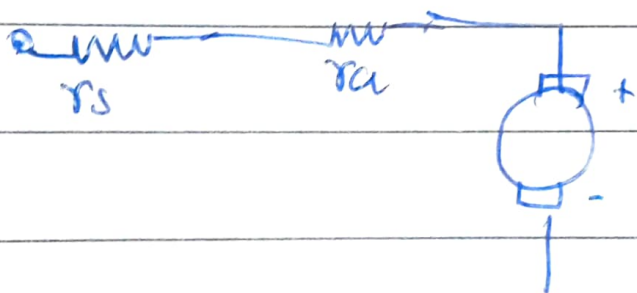

$$400 = \frac{V - I_a R_a}{\omega}$$

$$\Rightarrow K\phi = 3.62$$

i) At full load

$$\rightarrow A_{arm} = 25A$$

$$\Rightarrow E_b = V - I_a R_a'$$

$$\Rightarrow = \frac{120}{260} = 395.736 \text{ rpm}$$

ii)

At $\frac{1}{2}$ I_a

$$L = 1.51.28 \text{ rpm}$$

(3) FL T_a $T = 100 \text{ Nm}$

$$V = 240V$$

$$g_m \text{ w/o Load} = 1595 \text{ rpm} = 167.0.8$$

$$\text{at full } L = 1195 \text{ rpm} = 173.14 \text{ rad/s}$$

g) No Load

$$\omega = \frac{V}{K_e} \Rightarrow K_e = \frac{V}{\omega_{n.l.}} = \frac{240}{167.0.8}$$

$$\text{at full load } \omega = 1.4319$$

$$= 125.1401$$

$$\Rightarrow \text{Back emf} = K_e \omega = 1.4319 \times 125.14$$

$$= 179.39 \text{ V}$$

Armature circuit eq $\Rightarrow V = I_a K_e + E_b$

$$I_a = \frac{I}{K_e} = \frac{100}{1.4319} = 69.35$$

$$\text{From } R_a = \frac{V - E_b}{I_a} = \frac{240 - 179}{69.35} = 0.8658 \Omega$$

$$\downarrow) \text{ New vol } V = 0.833 \times 240 = 200V$$

$$N_g = 1 = 0.66 \text{ } 1.5 = 0.95$$

4.1

10kW, 250V, 1200 rpm

$$R_a = 0.2 \Omega$$

$$R_f = 120 \Omega$$

Full load = 80%

At full load: Output po
- 10kW

$$\Rightarrow \text{Input power } P_i = 12.5 \text{ kW}$$

$$P_m = 12.5 \text{ kW} = VI$$

$$\text{Input line current} = 50A$$

$$I_{\text{field}} = 2A$$

$$\Rightarrow \text{Armature current } I_a = I - I_f = 48A$$

Speed torque equation

$$\omega = \frac{V}{k_e} - \frac{E_b}{k_e k_f}$$

At

$$\Rightarrow 75\% \text{ of speed } \Rightarrow \omega = 0.75 \times 2\pi \times 1200$$

$$= 94.24 \text{ rad/s}$$

$$V = 250V$$

now R_e

at rated condition,

$$\omega = 1200 \text{ rpm} = 125.6637$$

$$I_a = 48A, R_a = 0.2\Omega$$

$$\Rightarrow E_b = V - I_a R_a = 250 - (48 \times 0.2) = 240.4V$$

$$\Rightarrow K_e = \frac{E_b}{\omega} = \frac{240.4}{125.6637} = 1.9170 \text{ V/rad}$$

\underline{P}

5) P (shunt motor) : $V = 250V$

$$R_a = 0.2\Omega$$

$$R_f = 100\Omega$$

While run at 600rpm, current drawn from supply $\equiv 60A$

$$I = 60A$$

$$\text{Field } I_f = \frac{V}{R_f} = \frac{250}{100} = 2.5A$$

$$\Rightarrow I_a = 60 - 2.5 = 57.5A$$

At 600rpm,

$$\omega = \frac{2\pi \times 600}{60} = 62.8318 \text{ rad/s}$$

$$E_b = V - I_a R_a$$

$$= 250 - (57.5 \times 0.2) = 238.5V$$

$$K_e = \frac{E_b}{\omega} = \frac{238.5}{62.8318} = 3.7955 \text{ V/rad}$$

$$E_{arm} = K_e I_a = 3.7958 \times 51 \text{ T} = 218.7813 \text{ V/m}$$

Now speed needs to be increased to

$$\omega = \frac{2\pi \times 800}{60} = 83.7778 \text{ rad/s}$$

adding

extra resistance in field circuit
(Load torque = constant)

$$\omega = \frac{V}{K_e} - \frac{R_{ef}}{K_e K_t} T$$

We know that, $K_e \propto I_a \Rightarrow K_e \propto \frac{V}{R_f}$

$$K_e' = K_e'$$

at 800 rpm

$$83.7778 = \frac{250}{K_e'} - \frac{0.2 \times 218.7813}{(K_e')}$$

$$\Rightarrow K_e' = 2.7979$$

$$\frac{K_e'}{R_f} = \frac{K_e''}{R_f} \Rightarrow R_f' = 135.108$$

$$\text{Additional current} \approx 135.108 - 100 \\ = 35.608 \text{ A}$$

c) 200V DC shunt motor

$$T = 105 \text{ Nm}$$

$$\text{at } \omega = 210 \text{ rpm}$$

$$\text{armature current} = 36 \text{ A}$$

$$F.C. = 1 \text{ A}$$

$$I_a = 37 \text{ A}$$

$$\text{at } 210 \text{ rpm, } V = 200 \text{ V}$$

$$E_b = V - I_a R_a = 200 - 37 \times 0.5 = 181.25 \text{ V}$$

Now speed

$$\omega = \frac{V - R_a I_a}{K_e}$$

$$210 \times \frac{2\pi}{60} = \frac{200 - 0.5 \times 37}{K_e}$$

$$\Rightarrow K_e = 2.26 \text{ V/rad/s}$$

$$\text{Percentage reduction} = \frac{E_b - E_b'}{E_b}$$

$$= \frac{181.25 - 2.26 \times \omega'}{181.25}$$

$$\Rightarrow \frac{R_a}{R_a'} = \frac{K_e}{K_e'} \Rightarrow R_a' = 332.3 \text{ m}\Omega$$

$$\text{Extra } R_a = 332.3 \text{ m}\Omega - 250 \text{ m}\Omega = 82.3 \text{ m}\Omega$$

Tutorial-7

Q for a sum $V_a = I_a R_a + I_a R_f + k \omega$

$$\Rightarrow V_a = I_a (R_a + R_f + k \omega) \quad (1)$$

$$\text{Torque } T_e = k I_a \quad (2)$$

Given data: 200V DC shunt motor

$$N = 700 \text{ rpm} \Rightarrow \omega = 2\pi \times 700$$
$$= 773.25 \text{ rad/s}$$

$$I_a = 20 \text{ A}$$

$$R_a + R_f = 0.5 \Omega$$

From this data,

$$V_a = I_a (R_a + R_f + k \omega)$$

$$\Rightarrow k = 0.1296 \text{ V/rad/s}$$

q) When load torque run by 1.45 times

$$\Rightarrow T_e' = 1.45 T_e$$

$$\Rightarrow I_a' = 1.2 T_e \text{ from (2)}$$
$$= 1.2 \times 20 = 24 \text{ A}$$

$$(1) \Rightarrow 200 = 24(0.5 + 0.1296 \omega)$$

$$\omega = 10.44$$

$$\omega \text{ rad} = 577.19 \text{ rpm}$$

(1)

$$I_a = 19A$$

① $\omega = 1000 \text{ rpm}$ (for 1st part)

$$\omega = 1000 \times \frac{2\pi}{60} \text{ rad/s}$$

$$= 104.72 \text{ rad/s}$$

②

(2) 220V DC motor motor is 220V

$$V = 220V$$

$$R_a = 0.8 \Omega \quad V_f = 0.1V \Rightarrow V = 0.1V$$

$$V_{brush} = 0.6V$$

For given data

$$V_a = I_a R_a + I_a R_f + k \omega + V_{brush}$$

$$\Rightarrow V_a = I_a (R_a + R_f) + V_{brush} \quad \text{--- (1)}$$

$$\Rightarrow 220 = 381.06 + k \times 628.3 \quad \text{--- (2)}$$

$$\Rightarrow k = 0.0813 \text{ N/A/rad/s}$$

a) when $I_a = 19A$

$$\Rightarrow 220 = 19 (0.6 + 0.0813 \omega) + 3$$

$$\Rightarrow \omega = 133.0 \text{ rad/s} = 1271 \text{ rpm}$$

$$S/I_a = 1$$

$$\text{use (1)} \Rightarrow \omega = 2661.7466 \text{ rad/s} = 25413.2 \text{ rpm}$$

c) Developed power $= E_b I_a = k I_a \omega I_a = k I_a^2 \omega$

Case (9) Developed power $= 0.0813 \times 19^2 \times 133.0$

$$= 751.5 \text{ W}$$

8/ Given data: 450V DC series motor;
 $R_a + R_f = 0.8 \Omega$

$$P_{\text{at full speed}} = 83.7718 \text{ W} - 1$$

$$\text{At rated torque} \Rightarrow I_a = 110 \text{ A}$$

9/

$$V_a = I_a R'$$

$$\Rightarrow R' = \frac{V_a}{I_a} = \frac{450}{110} = 4 \Omega$$

$$R = 3.2 \Omega$$

1/ At 600 rpm

$$\Rightarrow 450 = 110(R' + 0.0382 \times 60 \times 0.8318)$$

$$R' = 1.6 \Omega$$

$$R_{\text{total}} = 0.8 \Omega$$

4) At no load, terminal voltage = Induced emf = E_b

$$E_b = K \phi \omega$$


In other words $E_b \propto I_f \omega$

$$\frac{E_{b2}}{E_{b1}} = \frac{\omega_2}{\omega_1} \left(\frac{I_{f2}}{I_{f1}} \right) \Rightarrow E_{b2} = E_{b1} \left(\frac{\omega_2}{\omega_1} \right) \left(\frac{I_{f2}}{I_{f1}} \right)$$

9) $E_{b2} = 110 \times \frac{2.5}{2} = 137.5 \text{ V}$

5) $E_{b1} = 120 \times \left(\frac{1300}{1500} \right) \times \frac{2.3}{2} = 159.04 \text{ V}$

5) DC shunt generator

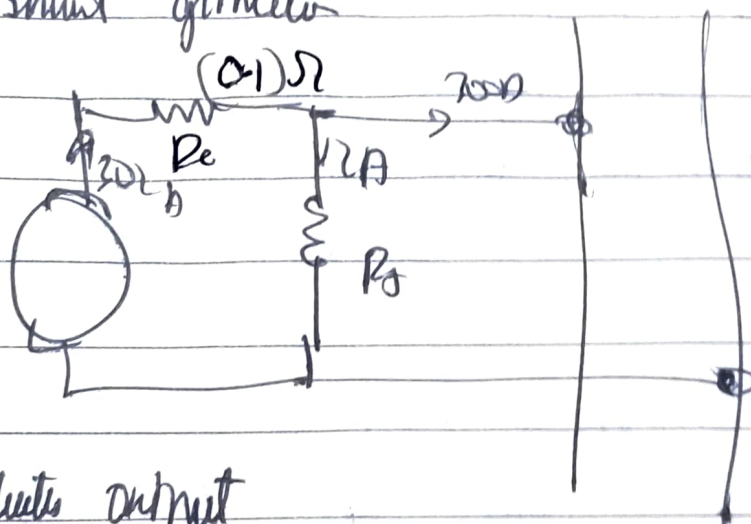

Delivered electric output

$P_{out} = 60 \text{ kW} @ 200 \text{ V}$

$\Rightarrow I = \frac{60 \times 10^3}{200} = 300 \text{ A}$

Field current $I_f = \frac{200}{100} = 2 \text{ A}$

Armature current $\approx I_a = 302$

Given $V_{brush} = 2V$

$\Rightarrow E_b = V + I_a R_a + V_{brush}$ (Generated equation)

$\Rightarrow E_b = 200 + (22 \times 0.1) + 2 = 232.2V = K\omega$

Therefore, $K = \frac{232.2}{2\pi \times 500} = 4.534 \text{ V rad s}^{-1}$

Now machine's prime mover input supply is removed while removed electrical terminals being connected to DC lines.

\Rightarrow field is energized & armature also

\Rightarrow Operates as motor

$P_m = \text{Input power} = VI$

$\Rightarrow I = \frac{5 \times 10^2}{200} = 25A$

$I_f = 2A$

$I_a = I - I_f = 25A - 2A = 23A$

$V_a = I_a R_a + E_b + V_{brush}$

$\Rightarrow E_b = V_a - I_a R_a - V_{brush}$
 $= 200 - (23 \times 0.1) - 2$

$= 217.7V$


Speed $\omega = \frac{217.7}{4.534} = 48.02 \text{ rad s}^{-1} = 471.5 \text{ rpm}$

1) DC shunt generator supplies load power of

10 kW at 250 V,

$$\Rightarrow V I = 10 \times 10^3$$
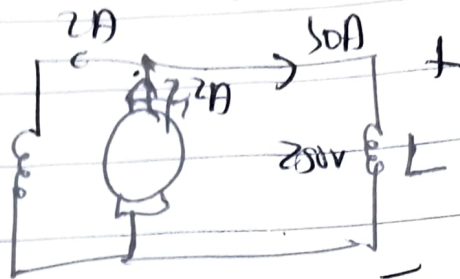
$$\Rightarrow I = \frac{10 \times 10^3}{250} = 40 \text{ A}$$



$$I_f = \frac{V_t}{R_f} = 2 \text{ A}$$

$$I_a = I + I_f = 42 \text{ A}$$

$$\text{Armature copper loss} = 1323 \text{ W}$$

$$\text{Iron + mechanical loss} = 600 \text{ W}$$

$$\Rightarrow \text{In power loss} = 1923 \text{ W}$$

$$\Rightarrow \text{Efficiency } \eta = 80.5\%$$

Q/ a) Given that full $I_f = 0.8 \text{ A}$

$$E_g = 115 \text{ V (from table)}$$

$$\text{If } K_{ev} = 115 \text{ V} \Rightarrow K_e = \frac{115}{\frac{25 \times 1200}{60}} = 0.60 \text{ V/rad}$$

$$P_a = 51.08 \text{ A} \times 250 \text{ V} = 12770.25 \text{ W}$$